Homework 1

Mitchel Fields

February 3, 2016

2.2 (b)
$$(x+y)(x+\overline{y}) = x(y+\overline{y}) = x(1) = x$$

(c)
$$xyz + \overline{x}y + xy\overline{z} = y(xz + \overline{x} + x\overline{z}) = y(\overline{x} + x(z + \overline{z})) = y(\overline{x} + x(1)) = y(1) = y$$

(d)
$$(A+B)(\overline{A}+\overline{B}) = (A+B)(\overline{AB}) = A\overline{B} + \overline{A}B = A \oplus B$$

(e)
$$(a+b+\overline{c})(\overline{a}.\overline{b}+c)=(a+b+\overline{c})(\overline{a+b}+c)=(a+b)\oplus c$$

(f)
$$\overline{a}bc + ab\overline{c} + abc + \overline{a}b\overline{c} = b(\overline{a}c + a\overline{c} + ac + \overline{a}\overline{c}) = b(1) = b$$

- 2.10 (a) The Boolean function $E = F_1 + F_2$ is true when either F_1 or F_2 or both are true. Thus it contains the union of their minterm sets.
 - (b) The Boolean function $G = F_1F_2$ is true only when both F_1 and F_2 are true. Thus it contains the intersection of their minterm sets.

2.11 (a)
$$F = xy + x\overline{y} + \overline{y}z$$

\ /				,							
	\boldsymbol{x}	y	z	xy	$x\overline{y}$	$\overline{y}z$	$xy + x\overline{y} + \overline{y}z$				
	0	0	0	0	0	0	0				
	0	0	1	0	0	1	1				
	0	1	0	0	0	0	0				
	0	1	1	0	0	0	0				
	1	0	0	0	1	0	1				
	1	0	1	0	1	1	1				
	1	1	0	1	0	0	1				
	1	1	1	1	0	0	1				
(b) $F = bc + \overline{a}.\overline{c}$											

-		00 0.0							
	a	b	c	bc	$\overline{a}.\overline{c}$	$bc + \overline{a}.\overline{c}$			
	0	0	0	0	1	1			
	0	0	1	0	0	0			
	0	1	0	0	1	1			
	0	1	1	1	0	1			
	1	0	0	0	0	0			
	1	0	1	0	0	0			
	1	1	0	0	0	0			
	1	1	1	1	0	1			

2.14 (a) With AND, OR, and inverter gates

- (b) With OR and inverter gates
- (c) With AND and inverter gates