

Homework 5

Mitchel Fields

March 4, 2016

Part 1

S_n	S_{n+1}
S_0	S_1
S_1	S_2
S_2	S_3
S_3	S_4
S_4	S_5
S_5	S_2
S_6	S_7
S_7	S_6

8 states means 3 bits.

S_n	S_{n+1}
S_0	110
S_1	100
S_2	000
S_3	001
S_4	011
S_5	010
S_6	101
S_7	111

Q_2^n	Q_1^n	Q_0^n	Q_2^{n+1}	Q_1^{n+1}	Q_0^{n+1}
1	1	0	1	0	0
1	0	0	0	0	0
0	0	0	0	0	1
0	0	1	0	1	1
0	1	1	0	1	0
0	1	0	0	0	0
1	0	1	1	1	1
1	1	1	1	0	1

$$D_2 = Q_2(Q_1 + Q_0)$$

$$D_1 = Q_0(\overline{Q_1} + \overline{Q_2})$$

$$D_0 = \overline{Q_2} \cdot \overline{Q_1} + Q_2 Q_0$$

Q_2^n	Q_1^n	Q_0^n	R	Y	G
1	1	0	1	0	0
1	0	0	1	0	0
0	0	0	0	0	1
0	0	1	0	1	0
0	1	1	1	0	0
0	1	0	1	1	0
1	0	1	0	0	0
1	1	1	1	0	0

Python simulation:

```
Q2 = 1
Q1 = 1
Q0 = 1
```

```
def NOT( a ):
    return 1 - a
```

```
for step in range( 20 ):

```

```
    D2 = Q2 & (Q1 | Q0)
    D1 = Q0 & (NOT(Q2) | NOT(Q1))
    D0 = (NOT(Q2) & NOT(Q1)) | (Q2 & Q0)
    R = (Q2 & NOT(Q0)) | Q1
    Y = NOT(Q2) & (Q1 ^ Q0)
    G = NOT(Q2) & NOT(Q1) & NOT(Q0)
```

```
    print( "Q2_Q1_Q0=%d_%d_%d | R_Y_G=%d_%d_%d" %
           ( Q2, Q1, Q0, R, Y, G ) )
    input( ">" )
```


```
Q0 = D0
Q1 = D1
Q2 = D2
```

```

Q2 Q1 Q0 = 1 1 0 | R Y G = 1 0 0
>
Q2 Q1 Q0 = 1 0 0 | R Y G = 1 0 0
>
Q2 Q1 Q0 = 0 0 0 | R Y G = 0 0 1
>
Q2 Q1 Q0 = 0 0 1 | R Y G = 0 1 0
>
Q2 Q1 Q0 = 0 1 1 | R Y G = 1 0 0
>
Q2 Q1 Q0 = 0 1 0 | R Y G = 1 1 0
>
Q2 Q1 Q0 = 0 0 0 | R Y G = 0 0 1
>
Q2 Q1 Q0 = 0 0 1 | R Y G = 0 1 0
>
Q2 Q1 Q0 = 0 1 1 | R Y G = 1 0 0
>
Q2 Q1 Q0 = 0 1 0 | R Y G = 1 1 0
> ■

Q2 Q1 Q0 = 1 0 1 | R Y G = 0 0 0
>
Q2 Q1 Q0 = 1 1 1 | R Y G = 1 0 0
>
Q2 Q1 Q0 = 1 0 1 | R Y G = 0 0 0
>
Q2 Q1 Q0 = 1 1 1 | R Y G = 1 0 0
>
Q2 Q1 Q0 = 1 0 1 | R Y G = 0 0 0
>
Q2 Q1 Q0 = 1 1 1 | R Y G = 1 0 0
>
Q2 Q1 Q0 = 1 0 1 | R Y G = 0 0 0
> ■

```

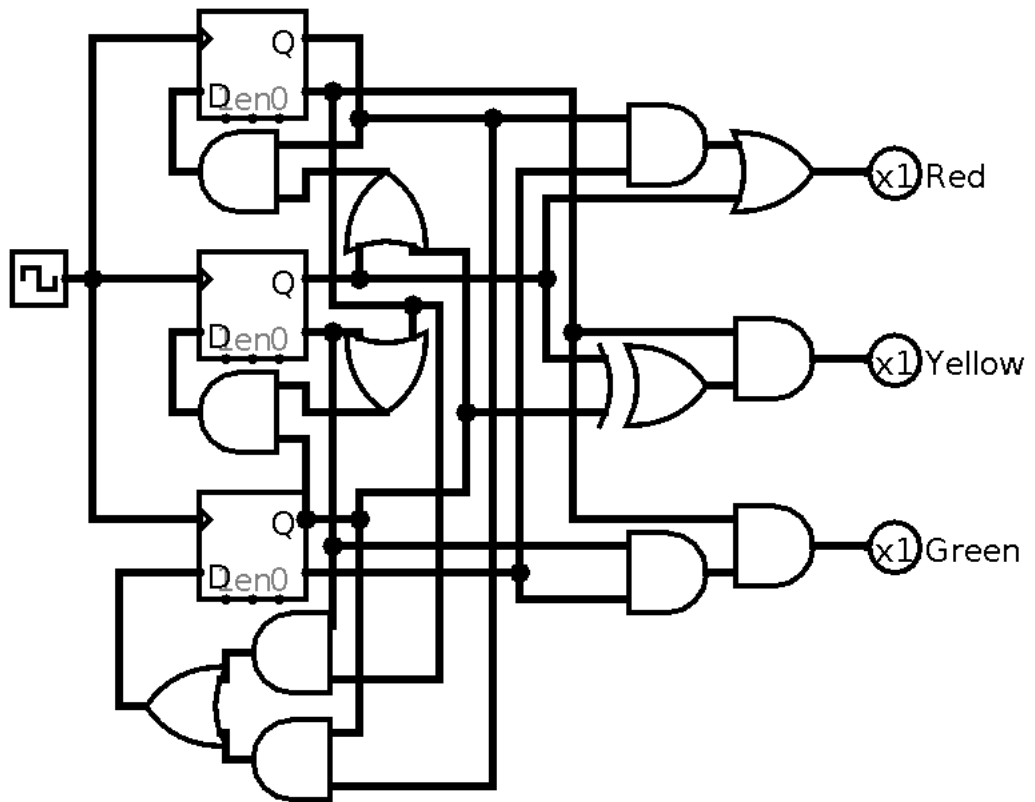

Part 2

There are 4 ways to connect S_6 or S_7 to another state by changing only one bit: $101 \rightarrow 100$, $101 \rightarrow 001$, $111 \rightarrow 110$, and $111 \rightarrow 011$

Of these options, only $101 \rightarrow 001$ reduces the number of covers in a Karnaugh map of the affected bits.

D_2

		Q_1Q_0			
		00	01	11	10
Q_2	0	0	0	0	0
	1	0	1	1	1

Becomes:

D_2

		Q_1Q_0			
		00	01	11	10
Q_2	0	0	0	0	0
	1	0	0	1	1

The result changes the equation for D_2 from $D_2 = Q_2(Q_1 + Q_0)$ to $D_2 = Q_2Q_1$. The adjusted circuit diagram is as follows:

