

# Homework 2

Mitchel Fields


February 9, 2016
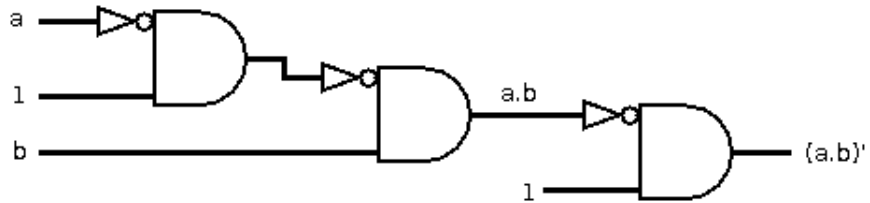
## Question 1

AND The AND gate configuration could be made universal. If  $b$  is always 1, the gate's output becomes  $\bar{a}$ .




Using one gate with inputs  $a$  and 1, a second taking the output of the first gate and  $b$ , and a third taking the second output and 1, the gate can be used to create a NAND gate, which is universal.



XOR The XOR configuration cannot be made universal. As it is, it has the following truth table.

$a$	$\bar{a}$	$b$	$\bar{a} \oplus b$
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	1

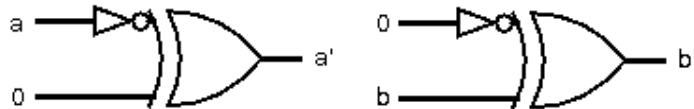This truth table is recognizable as XNOR. A NOT gate can be made if either input is held at 0.



Even with the addition of more NOT gates, the gate can only be made an XOR or XNOR.

$a$	$b$	$\bar{a}$	$\bar{b}$	$\bar{a} \oplus b$	$\bar{a} \oplus \bar{b}$	$\bar{\bar{a}} \oplus b$	$\bar{\bar{a}} \oplus \bar{b}$
0	0	1	1	1	0	0	0
0	1	1	0	0	1	1	1
1	0	0	1	0	1	1	1
1	1	0	0	1	0	0	0

As such, this gate cannot be made universal.

Question 2

$$f(a, b, c, d) = \Sigma(0, 1, 2, 3, 12, 13, 14, 15)$$

ab \ cd	00	01	11	10
00	1	0	1	0
01	1	0	1	0
11	1	0	1	0
10	1	0	1	0

$$f(a, b, c, d) = \bar{a}.\bar{b} + a.b = \overline{a \oplus b}$$

$$g(a, b, c, d) = \Sigma(0, 1, 2, 3, 4, 5, 6, 7, 8, 9, 10, 12, 13, 14, 15)$$

ab \ cd	00	01	11	10
00	1	1	1	1
01	1	1	1	1
11	1	1	1	0
10	1	1	1	1

$$g(a, b, c, d) = \overline{a.\bar{b}} + \bar{c} + c.\bar{d} = \bar{a} + b + \bar{c} + c.\bar{d}$$

$$h(a, b, c) = \Pi(0, 1, 2, 3)$$

		a	
		0	1
bc	00	0	1
	01	0	1
	11	0	1
	10	0	1

$$h(a, b, c) = a$$

$$k(a, b, c, d) = \Pi(0, 1, 7, 8)$$


		ab			
		00	01	11	10
cd	00	0	1	1	0
	01	0	1	1	1
	11	1	0	1	1
	10	1	1	1	1

$$\begin{aligned}
 k(a, b, c, d) &= b.\bar{c} + a.(c + d) + c.\bar{d} + c.\bar{a}.\bar{b} \\
 &= b.\bar{c} + a.c + a.d + c.(\bar{d} + \bar{a}.\bar{b}) \\
 &= a(c + d) + b.\bar{c} + c.(\bar{d} + \bar{a}.\bar{b})
 \end{aligned}$$


Question 3

a	b	c	majority voter
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

Active-High:

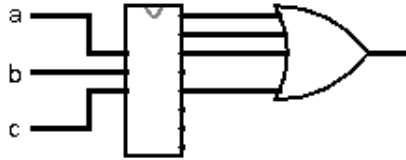

Active-Low with Active-Low Enable:

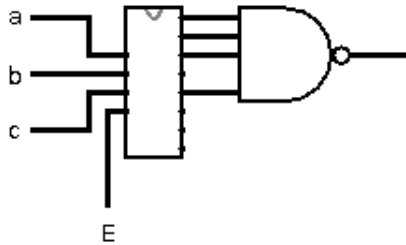

Question 4

```
def decoder(a,b,c,E):
    D0 = not a and not b and not c and E
    D1 = not a and not b and c and E
    D2 = not a and b and not c and E
    D3 = not a and b and c and E
    D4 = a and not b and not c and E
    D5 = a and not b and c and E
    D6 = a and b and not c and E
    D7 = a and b and c and E
    return [D0, D1, D2, D3, D4, D5, D6, D7]

def main():
    print( " _E_a_b_c_| _D7_D6_D5_D4_D3_D2_D1_D0" )
    print( "-----+-----" )
    for E in [ 0, 1 ]:
        for a in [ 0, 1 ]:
            for b in [ 0, 1 ]:
                for c in [ 0, 1 ]:
                    print( "%3d%3d%3d%3d_|" %
                        ( E, a, b, c ), end="" )
                    result = decoder(a, b, c, E)
                    result.reverse()
                    for D in result:
                        print( "%4d" % D, end="" )
                    print()
```

main()

E	a	b	c	D7	D6	D5	D4	D3	D2	D1	D0
0	0	0	1	0	0	0	0	0	0	0	0
0	0	0	0	0	0	0	0	0	0	0	0
0	0	1	0	0	0	0	0	0	0	0	0
0	0	1	1	0	0	0	0	0	0	0	0
0	1	0	0	0	0	0	0	0	0	0	0
0	1	0	1	0	0	0	0	0	0	0	0
0	1	1	0	0	0	0	0	0	0	0	0
0	1	1	1	0	0	0	0	0	0	0	0
1	0	0	0	0	0	0	0	0	0	0	1
1	0	0	1	0	0	0	0	0	0	1	0
1	0	1	0	0	0	0	0	0	1	0	0
1	0	1	1	0	0	0	0	1	0	0	0
1	1	0	0	0	0	0	1	0	0	0	0
1	1	0	1	0	0	1	0	0	0	0	0
1	1	1	0	0	1	0	0	0	0	0	0
1	1	1	1	1	0	0	0	0	0	0	0